

Digital circuits.

Boolean algebra & logic gates ('0' & '1')
→ Cost of the circuit.
→ Simple realization of a circuit.

* George Boole : → developed an algebraic system (Boolean algebra)

→ OR (+) @ 1' @ U @ V } binary operators.
→ AND (.) @ 1 @ & @ && }
→ NOT. or inverter → unary operators.

→ In boolean algebra:

$$A + A = A$$

$$A \cdot A = A$$

→ In ordinary algebra

$$A + A = 2A$$

$$A \cdot A = A^2$$

→ In binary no system

$$1 + 1 = (10)$$

$$1 \cdot 1 = 1$$

Axioms & postulates.

$$x + 0 = x$$

$$x + 1 = 1$$

$$x + x = x$$

$$x + \bar{x} = 1$$

$$(\bar{\bar{x}}) \text{ or } (x')' = x$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot \bar{x} = 0$$

OR operation (logical addition)
AND operation (logical multiplication)

1. Commutative law : $x + y = y + x$ | $x \cdot y = y \cdot x$.
2. Associative law : $x + (y + z) = (x + y) + z$
 $x \cdot (y \cdot z) = (x \cdot y) \cdot z$
3. Distributive law :

(i) $x(y + z) = xy + xz$.

(ii) $x + yz = (x + y)(x + z)$

Absorption theorem:

1. $x + xy = x$.

$\rightarrow x(1 + y) = x \cdot 1 = \underline{x}$

$A + BC = (A + B)(A + C)$

2. $x + \bar{x}y = x + y$.


$(x + \bar{x})(x + y)$

MUX to logic gates:

1. NAND, NOR - Universal gate.

* MUX \rightarrow Universal logic.

2:1 MUX

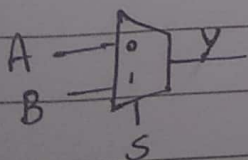


$2^n = \text{inputs}$.

$n \rightarrow \text{selection lines}$.

<u>S</u>	<u>Y</u>
0	A
1	B

$Y = A\bar{S} + BS$.


Inverter Design:

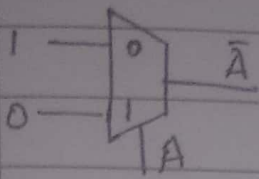

$$y = 1 \cdot \bar{A} + 0 \cdot A$$

$$y = \bar{A}$$


AND gate using MUX.

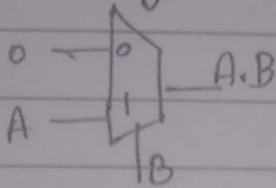


$$y = 0 \cdot \bar{B} + A \cdot B$$

$$y = A \cdot B$$


OR gate.

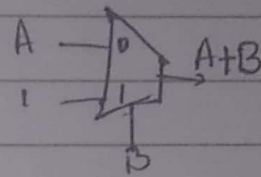

XOR

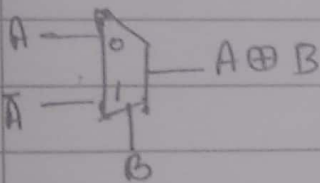

Ex-NOX

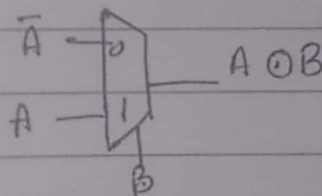

BCD to 7-segment decoder.

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

